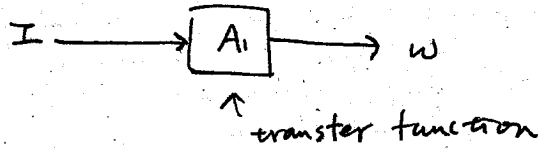


open-loop control


ex: Fan

if $\omega = A_1 \cdot I$
 ↑ angular velocity ↑ current



∴ ω may change with time because motor may heat up and alter the performance (A_1 may change)
 → common problem for open-loop control

Feed back Control

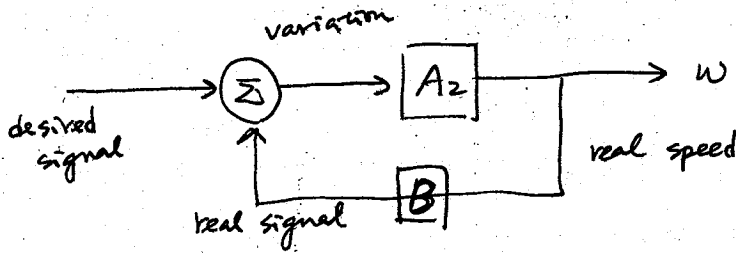

example: circuit




$V_o = AV_s$

$dV_o = A dV_s + V_s dA$

$= V_s dA$

$\frac{dV_o}{V_o} = \frac{dA}{A}$

→ if A changes 1%, V_o changes 1%

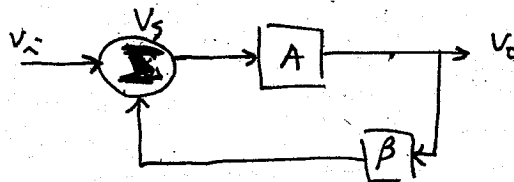

$V_o = AV_s = A(V_i + \beta V_o)$

$V_o(1 - A\beta) = AV_i$

$A_f = \frac{V_o}{V_i} = \frac{A}{1 - A\beta}$ ← close-loop gain

e.g. 741 amplifier $A \approx 2 \times 10^5$
 if $\beta = -0.1$

→ $A_f = \frac{2 \times 10^5}{1 - 2 \times 10^5(-0.1)} \approx 10$

→ if A change +1% ⇒ $A_f = 9.9995$



if A is huge

$$A_f \approx \frac{A}{-A\beta} = -\frac{1}{\beta} \quad V_o = A_f V_i = \frac{A}{1-A\beta} V_i$$


derive yourself

$$\rightarrow \frac{dV_o}{V_o} = \frac{dA}{A} \cdot \frac{1}{(1-A\beta)}$$

A changes 1% \Rightarrow V_o changes 0.005%

however, the gain changes from 2×10^5
 \rightarrow only 10

• Amplifier (ex/voltage amplifier)

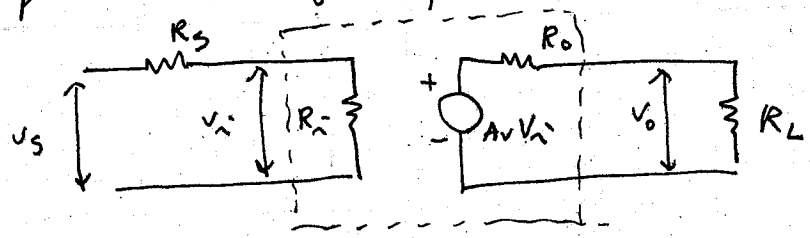

voltage amplifier

$$V_i = V_s \frac{R_i}{R_i + R_s} \quad \text{better } R_i \gg R_s \rightarrow V_i \approx V_s$$

* no reduction ~~in~~ at the input

$$V_o = A_v V_i \cdot \frac{R_L}{R_o + R_L} \quad \text{better } R_o \ll R_L \rightarrow V_o \approx A_v V_i \approx A_v V_s$$

ex/ HP equipment $R_i \approx 1 M\Omega$
 $R_o \approx 50 \Omega$

same on current amplifier \rightarrow small R_i
 big R_o

Ideal Amplifiers



741
 $R_{in} > 2 M\Omega$ ($I_m \approx 80 \text{ nA}$)
 $\text{Gain} \approx 2 \times 10^5$ (low frequency)


circuit analysis can assume

$$\begin{cases} R_{in} = \infty \\ \text{Gain} = \infty \end{cases}$$

& check

$$\rightarrow \begin{cases} I_{in} = 0 & \because R_{in} = \infty \\ V_+ - V_- = 0 & \because V_{out} = G \cdot (V_+ - V_-) \end{cases}$$

example = inverting amplifier

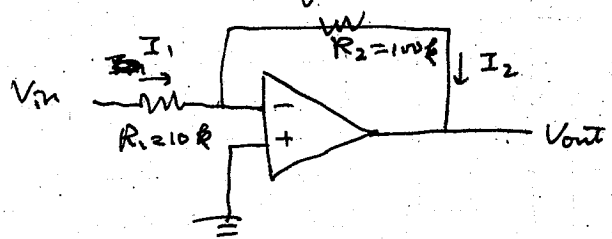

$$\begin{aligned} ① \quad I_{in} &= 0 \\ &\Rightarrow I_1 \approx I_2 \\ ② \quad V_+ - V_- &= 0 \Rightarrow V_+ \approx V_- = 0 \\ I_2 = I_1 &= \frac{V_{in}}{R_1} \\ V_{out} &= 0 - I_2 R_2 = -\frac{R_2}{R_1} V_{in} \end{aligned}$$


$$Gain = -\frac{R_2}{R_1} = -10$$

check assumption

$$\begin{aligned} \text{if } V_{in} &= 0.5V \\ I_1 &= \frac{0.5}{10k} = 50 \mu A \gg 80nA \quad \text{OK} \\ V_{out} = -5V &\Rightarrow V_+ - V_- = \frac{-5}{2 \times 10^5} \\ &= 2.5 \times 10^{-5} \approx 0 \quad \text{OK} \end{aligned}$$

real examples

• non-inverting amplifier

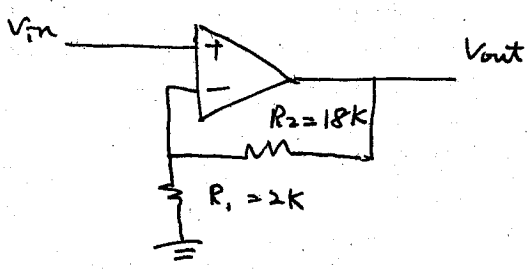

$$\begin{aligned} V_{in} = V_+ = V_- = V_{out} \cdot \frac{R_1}{R_1 + R_2} \\ \frac{V_{out}}{V_{in}} &= 1 + \frac{R_2}{R_1} \\ &= 10 \end{aligned}$$

if $R_2 = 0 \Rightarrow \frac{V_{out}}{V_{in}} = 1$
voltage follower

22-141 50 SHEETS
22-142 100 SHEETS
22-144 200 SHEETS

